

Simulim 22  
Ayush Agarwal  
20095021  
Electronics (ECE)

2)

i) When the load is purely resistive, the diodes do not conduct.

The voltage will be  $+V_{dc}$  while the ~~input~~  $\theta_1$  &  $\theta_2$  are switched on, whereas it will be  $-V_{dc}$  when  $\theta_3$  &  $\theta_4$  are switched on.

$$V_o = \begin{matrix} +V_{dc} & \theta_1, \theta_2 \text{ on} \\ -V_{dc} & \theta_3, \theta_4 \text{ on} \end{matrix}$$

$$V_o^2 = |V_{dc}|^2 \text{ both ways}$$

$$V_{RMS} = \sqrt{\frac{\int_0^T V^2 dt}{\int_0^T dt}} = |V| \text{ when } V \text{ const}$$

$$V_{RMS} = \frac{V_{dc}}{\sqrt{2}}$$



$$V_{RMS} = \sqrt{\frac{\int_0^{T/2} (+V_{dc})^2 dt + \int_{T/2}^T (-V_{dc})^2 dt}{\int_0^T dt}}$$

[120° means till  $T/3$ ]

$$V_{RMS} = V_{dc}$$

$$V_{RMS} = 300V$$


ii) Now  $R = 50 \Omega$ ,  $L = 10mH$

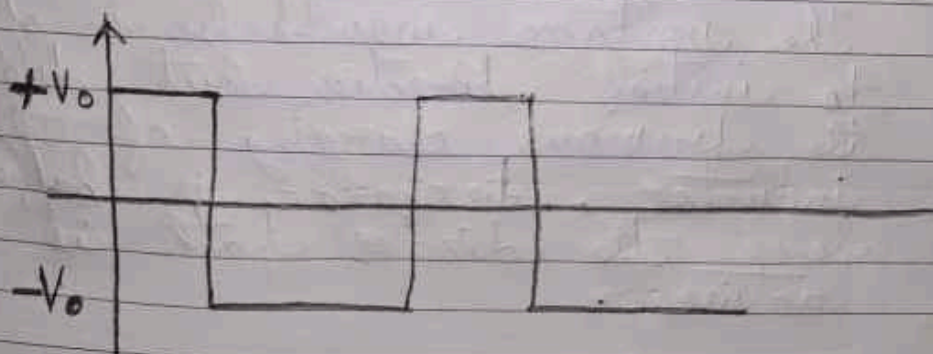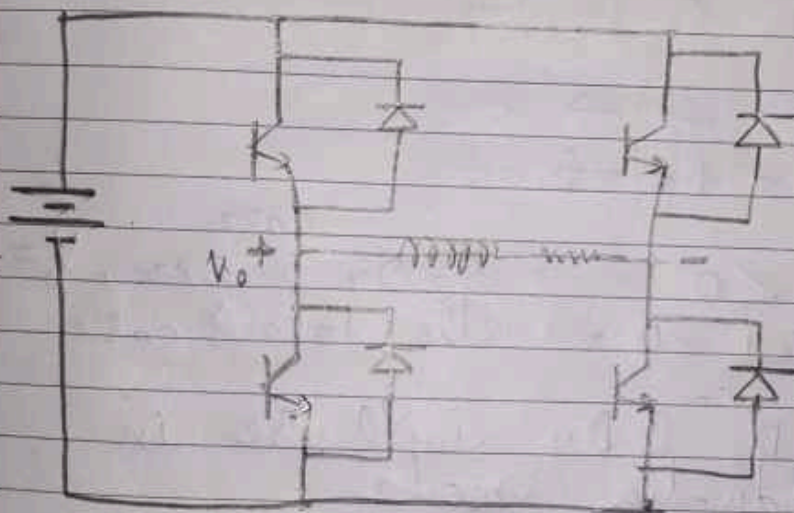

The output voltage is same, as that in case i so  
 $V_{RMS} = 300V$



(iii)

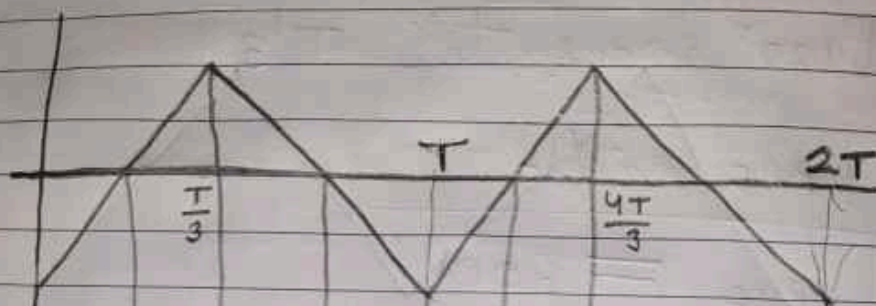

$D_1$	$\Theta_1$	$D_3$	$\Theta_3$
$D_2$	$\Theta_2$	$D_4$	$\Theta_4$

$i$	$\leftarrow$	$\rightarrow$	$\rightarrow$	$\leftarrow$
$V$	$+-$	$+-$	$-+$	$-+$

$V_{out} < 0 \rightarrow$  <sup>case</sup>  $\Theta_3 \Theta_4$  active,  $V_o = -V_c$   
&  $I_{out} > 0 \rightarrow$  the diodes case

$\therefore D_3$  &  $D_4$  will be in conduction mode

The voltage would be in off to initial direction but due to the previous charging of the inductor, discharge is happening hence the diodes path is active.

Ayush Agarwal  
20075021  
Electronics

