

Simulim 22

Ayush Agarwal 20095021
Electronics (ECE)

4) Buck Converter

$$V_i = 60V \quad V_o = 25$$

$$f = 25 \text{ kHz} = f$$

We know that
Duty cycle $D = \frac{V_o}{V_i}$

$$\therefore D = \frac{25}{60} = \frac{5}{12} \approx 0.4167$$

$$D \approx 0.42$$

We also know that

$$L_{\min} = \frac{(1-D)R}{2f}$$

$$\therefore L_{\min} = \frac{(1-0.4167)R}{2 \times 25 \times 10^3}$$

$$\frac{0.5833}{50} \times 10^{-3} \times R$$

$$L_{\min} \approx (11.66) R$$

\therefore for precaution we take L 25% greater than calculated

$$\therefore L = 1.25 \times 11.66 \times R$$

$$L = 14.58 R$$

$$Q \quad C = \frac{1-D}{8L \left(\frac{\Delta V_o}{V_o} \right)^2 f^2}$$

$$\text{Let } \frac{\Delta V_o}{V_o} = x$$

$$C = \frac{0.5833}{8 \times 14.58 \times R \times x \times (25 \times 10^3)^2}$$

$$\frac{0.005}{R \times x \times 625 \times 10^6}$$

$$C = \frac{8 \times 10^{-6} \times 10^{-6}}{R \times x}$$

$$\text{Let } x = \frac{1}{1000} \quad \left[\begin{array}{l} \text{Meaning } 0.1\% \\ \text{max deviation} \\ \text{from required voltage} \\ \text{acceptable} \end{array} \right]$$

$$\text{Then } C = \frac{8 \times 10^{-9}}{R}$$

$$\text{Let } R = 8 \times 10^{-3} \Omega \quad [\text{just an example}]$$


$$\text{Then } L = 14.58 \times 8 \times 10^{-3} \text{ H}$$

$$L = 116.64 \text{ mH}$$

$$C = \frac{8 \times 10^{-9}}{8 \times 10^{-3}} = 10^{-6}$$

$$C = 1 \mu F$$

∴ the circuit would be

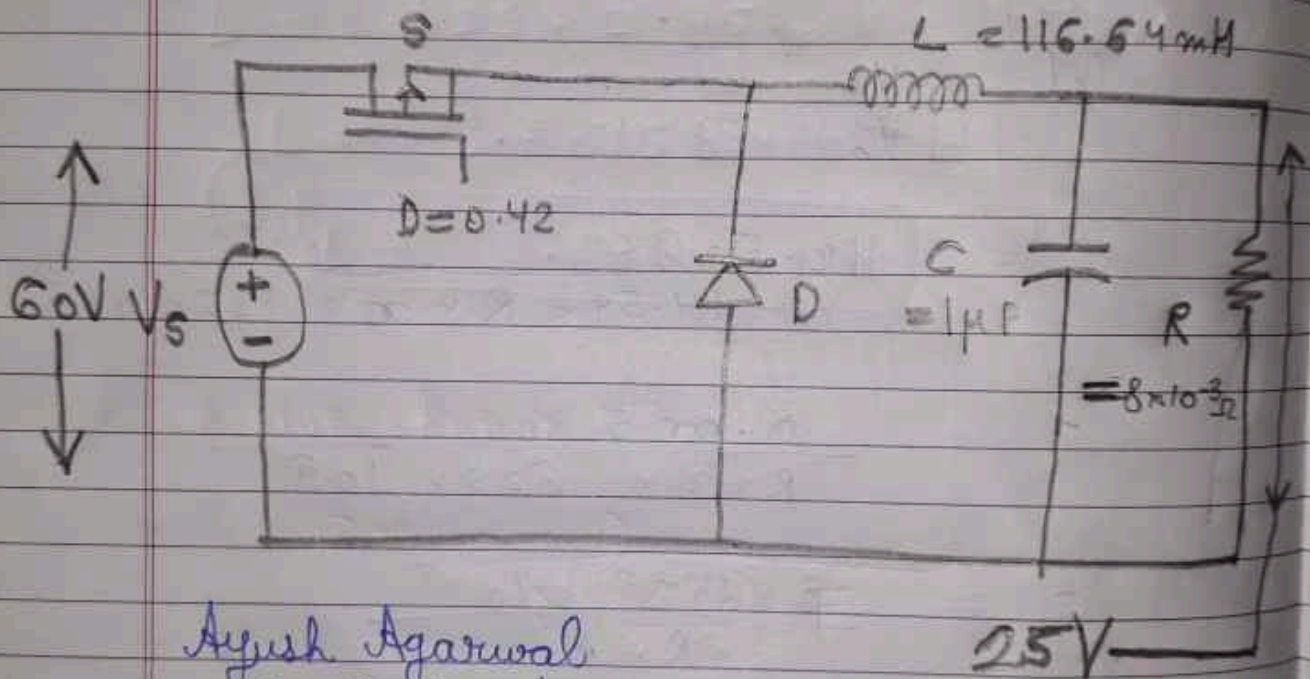

Ayush Agarwal
2009 5021
Electronics